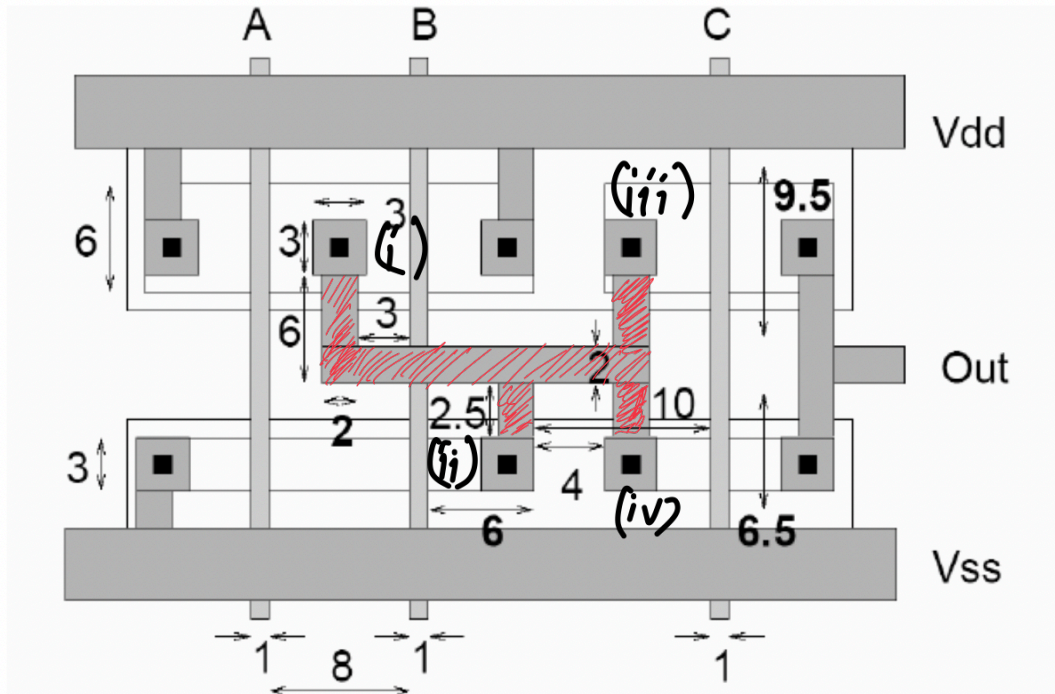


# HW Question 1

Estimate the total capacitance at the output of the NAND gate in the following layout. All dimensions are in microns and drawn to scale. Assume that  $C_{ja} = 0.5 \text{ fF}/\mu\text{m}^2$  and  $C_{jp} = 0.45 \text{ fF}/\mu\text{m}$  for both n and p transistors. Consider only the parallel plate capacitance component of the interconnect capacitance and use the interconnect capacitance values given in the previous slide.



Solution:-

The output of the NAND gate is affected by the junctions at i, ii, iii and iv.

$$\text{So, total capacitance} = \text{Capacitance}_{jn}(i) + \text{Capacitance}_{jn}(ii) + \text{Capacitance}_{jn}(iii) + \text{Capacitance}_{jn}(iv) + \text{Interconnect capacitance}$$

$jn = \text{junction}$

$$(i) \text{ capacitance}_{jn} C(i) = C_{ja}(w_p \times y_p) + C_{jp}(2y_p)$$

Since  $A_{pmos}$  and  $B_{pmos}$  have same drain.

At junction (i),  $w_p = 6$ ,  $y_p = 8$

$$\therefore C(i) = (0.5)(48) + (0.45)(16)$$

$$\boxed{C(i) = 31.2 \text{ fF}} \rightarrow \textcircled{A}$$

Similarly for capacitance<sub>jn</sub>  $C(ii)$ ,  $w_n = 3$ ,  $y_n = 6$

$$\text{Using } C_{ja}(w y) + C_{jp}(2y + w)$$

$$C(ii) = (0.5)(18) + (0.45)(15)$$

$$\boxed{C(ii) = 15.75 \text{ fF}} \rightarrow \textcircled{B}$$

For  $C(iii)$ ,  $w_p = 6$  &  $y_p = 6$

$$C(iii) = (0.5)(36) + (0.45)(18)$$

$$\boxed{C(iii) = 26.1 \text{ fF}} \rightarrow \textcircled{C}$$

Uy for  $C(iv)$ ,  $\omega_{pn} = 3$  &  $\gamma_n = 6$

$$C(iv) = (0.5)(18) + (0.45)(15)$$

$$\boxed{C(iv) = 15.75 \text{ fF}} \rightarrow \textcircled{D}$$

we need to calculate interconnect capacitance for the shaded region (red) in the diagram.

Given, metal 1 over field oxide =  $0.03 \text{ fF}/\mu\text{m}^2$

metal 1 over poly =  $0.053 \text{ fF}/\mu\text{m}^2$

$$\begin{aligned} \therefore C(\text{interconnect}) &= (12)(0.030) + (6)(0.030) + \\ &\quad (21)(0.030) + (12)(0.030) + \\ &\quad (5)(0.030) + (5)(0.030) + \\ &\quad (0.053)(2) \end{aligned}$$

$$\begin{aligned} &= 0.36 + 0.18 + 0.63 + 0.36 + 0.15 \\ &\quad + 0.15 + 0.106 \end{aligned}$$

$$\boxed{C(\text{interconnect}) = 1.876 \text{ fF}} \rightarrow \textcircled{E}$$

$$\text{Output capacitance} = A + B + C + D + E$$

$$= 31.2 + 15.75 + 26.1 + 15.75 + 1.876.$$

$$\boxed{\text{Output capacitance} = 90.676 \text{ fF}}$$

