


Name: Keerthan Nandigama

SBU ID: 115375118

Email: keerthan.nandigama@stonybrook.edu

CAD Assignment 2

 
Objective: Design and verify a four-input parity generator consisting of three XOR gates in the 45 nm CMOS technology.




The nominal supply voltage is set to 1.1 Volts. The circuit should drive an external load of 12 fF in addition to the internal parasitic capacitances that exist in the circuit. Assume 50 ps of rise/fall times for your input signals.

Design constraints: The primary design objective is to minimize the power-delay product of the circuit for the input pattern provided below. Delay should correspond to the worst-case delay between input and output. Power should correspond to the average power consumption over 7 ns for the input pattern below. In the worst case, the circuit should have a propagation delay of no more than 200 ps.


Schematic of XOR gate

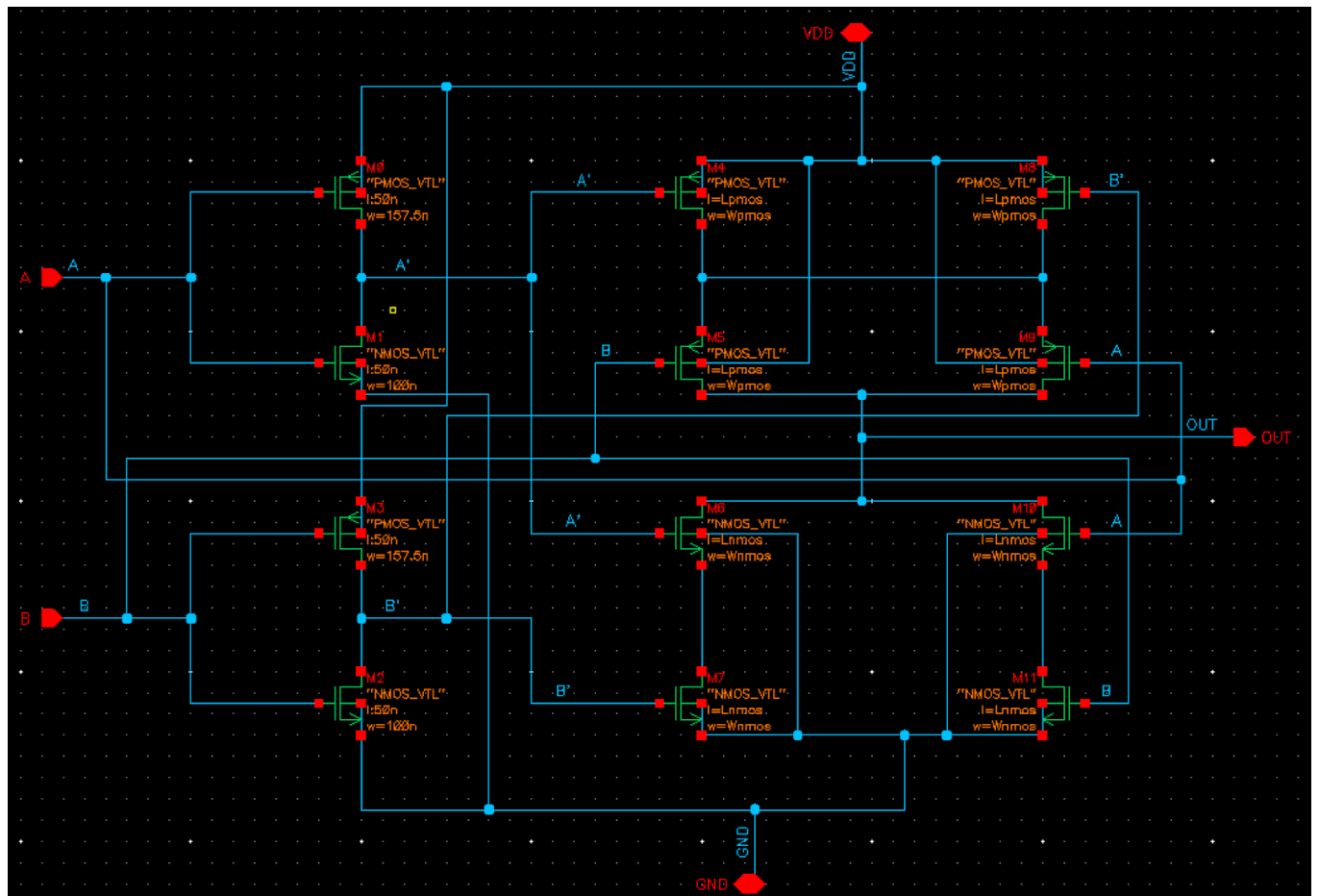

Symbol of XOR gate

 

Schematic view of parity generator

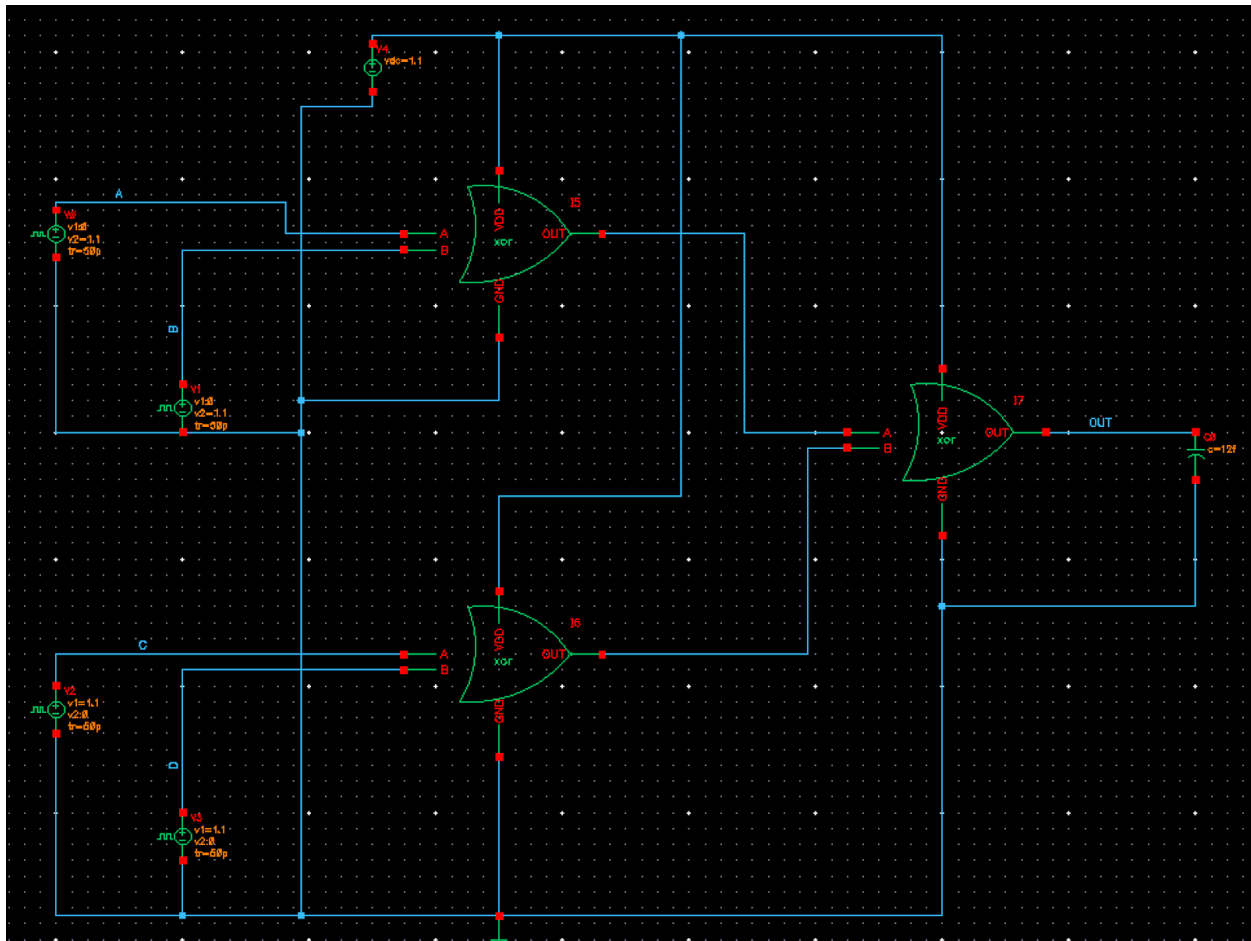

	Wnmos ▼	(delay(?w...e nil))/2	(average(...)) * 1.1)
1	100.0E-9	116.8E-12	-17.37E-6
2	116.7E-9	106.9E-12	-18.22E-6
3	133.3E-9	98.18E-12	-18.93E-6
4	150.0E-9	90.63E-12	-19.55E-6
5	166.7E-9	84.21E-12	-20.12E-6
6	183.3E-9	78.79E-12	-20.67E-6
7	200.0E-9	74.41E-12	-21.26E-6
8	216.7E-9	70.70E-12	-21.87E-6
9	233.3E-9	67.56E-12	-22.48E-6
10	250.0E-9	64.84E-12	-23.08E-6

The goal in designing a 4-bit parity generator is to minimize the power-delay product. This involves a tradeoff between reducing power consumption by decreasing parasitic capacitance and minimizing average propagation delay by increasing the W/L ratio of ON transistors. Transistor resizing is done by sweeping the NMOS width(Wnmos) from 100 nm to 250 nm while keeping the PMOS width (Wpmos) at 1.6 times of Wnmos and both transistor lengths are fixed at 50nm.

We're getting the minimum power-delay when Wnmos = 200 nm, therefore, Wpmos = 1.6 * 200 = 320 nm

Wnmos = 200 nm


Wpmos = 320 nm

Transient analysis waveform:




Average Propagation delay: **74.41 ps**

XOR Layout

 

Parity Generator Layout

 

Parity Generator DRC

FileViewHighlightToolsWindowSetup

Help


Search

Show AllNo Results Found


Check / Coll	Results
✓ Check Well.1	0
✓ Check Well.2	0
✓ Check Well.4	0
✓ Check Poly.1	0
✓ Check Poly.2	0
✓ Check Poly.3	0
✓ Check Poly.4	0
✓ Check Poly.5	0
✓ Check Poly.6	0
✓ Check Active.1	0
✓ Check Active.2	0
✓ Check Active.3	0
✓ Check Active.4	0
✓ Check Implant.1	0
✓ Check Implant.2	0
✓ Check Implant.3	0
✓ Check Implant.4	0
✓ Check Implant.6	0
✓ Check Contact.1	0
✓ Check Contact.2	0
✓ Check Contact.3	0
✓ Check Contact.4	0
✓ Check Contact.5	0
✓ Check Contact.6	0
✓ Check Metal.1.1	0
✓ Check Metal.1.2	0
✓ Check Metal.1.3	0
✓ Check Metal.1.4	0
✓ Check Via.1.1	0
✓ Check Via.1.2	0
✓ Check Via.1.3	0

Rule File Pathname: /home/xxxx/assignments/_calibre.drc
Well and Preill must not overlap

Parity Generator LVS

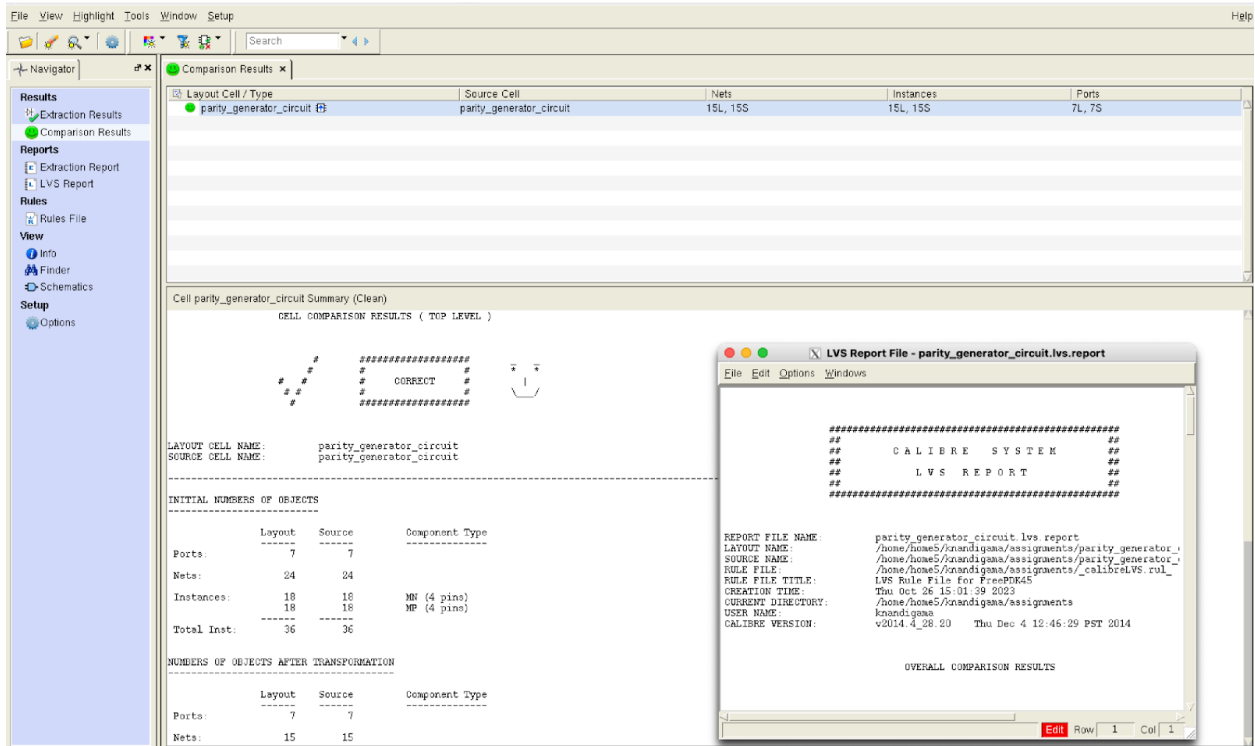

Post-layout simulation data

 


After observation, the worst case scenario is marked between the 4th input and the output.

Propagation delay for low to high: 116 ps

Propagation delay for high to low: 87.6 ps

 Average propagation delay: **101.8 ps** (less than the given constraint, 200 ps)



Average current is plotted on the graph which is **24.9 uA**.

Dynamic power = $V_{dd} \times \text{average current} = 1.1 \times 24.9 = \mathbf{27.39 \text{ micro watts}}$.

Power delay product = dynamic power * average propagation delay
 $= 27.39 \text{ micro} \times 101.8 \text{ pico} = \mathbf{2.7883 \text{ femto watt sec}}$